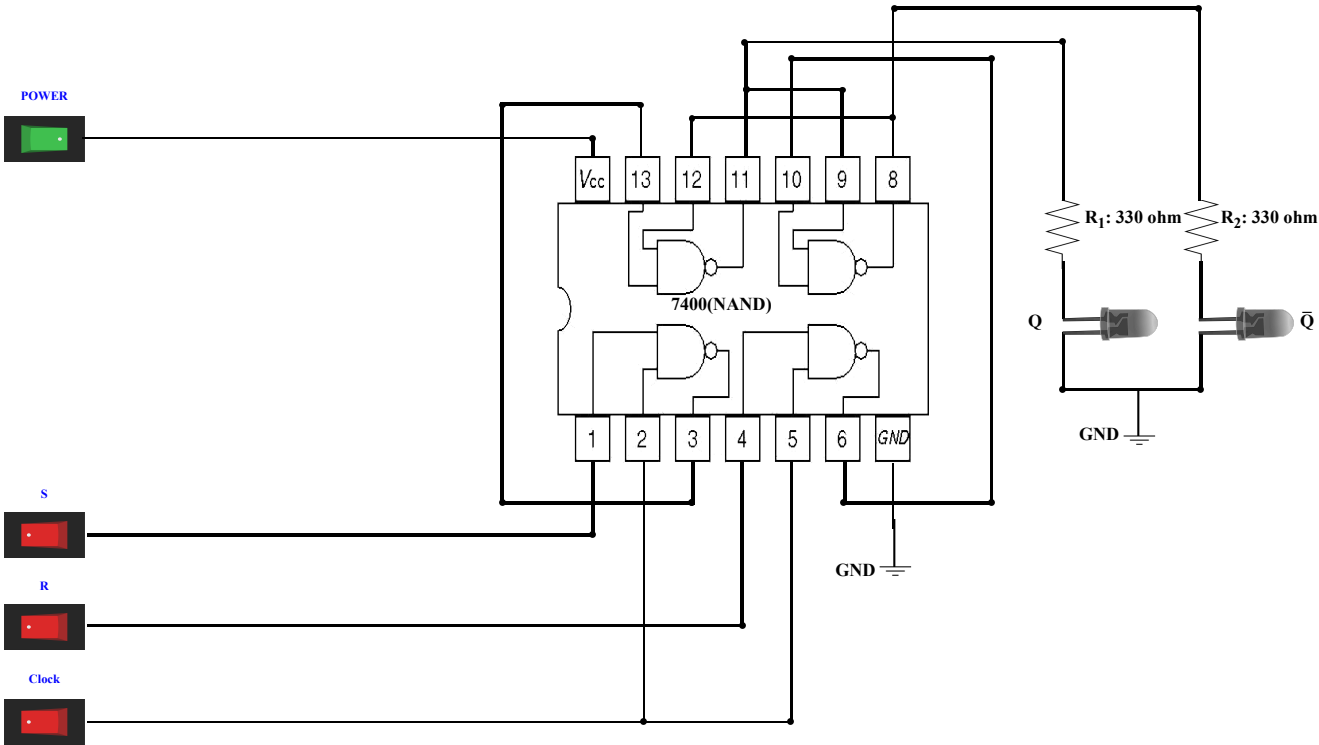


INSTRUCTIONS

Experiment to perform SR Flip Flop on kit



TRUTH TABLE								PRINT	Add
Serial No.	clock	S	R	Q(n-1)	Q̄(n-1)	Q	Q̄	Remark	
1	1	0	0	0	1	0	1	No change	
2	1	0	1	0	1	0	1	Reset	
3	1	1	0	0	1	1	0	set	
4	1	1	1	1	0	0	0	INVALID	

