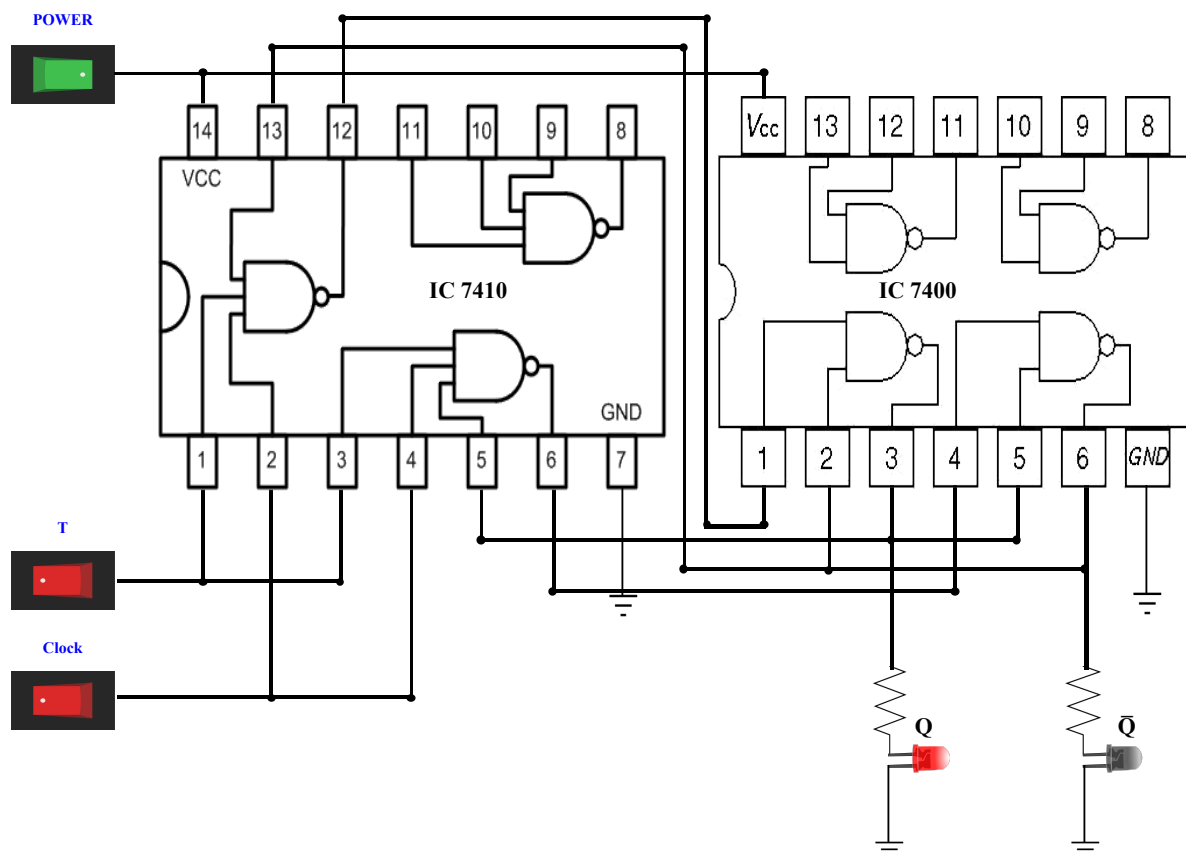


### Experiment to perform T Flip Flop on kit



TRUTH TABLE							Add	Print
Serial No.	Clock	T	$Q_{n-1}$	$\bar{Q}_{n-1}$	Q	$\bar{Q}$	Remarks	
1	1	0	x	x	0	1	No change	
2	1	1	0	1	1	0	Toggle	

