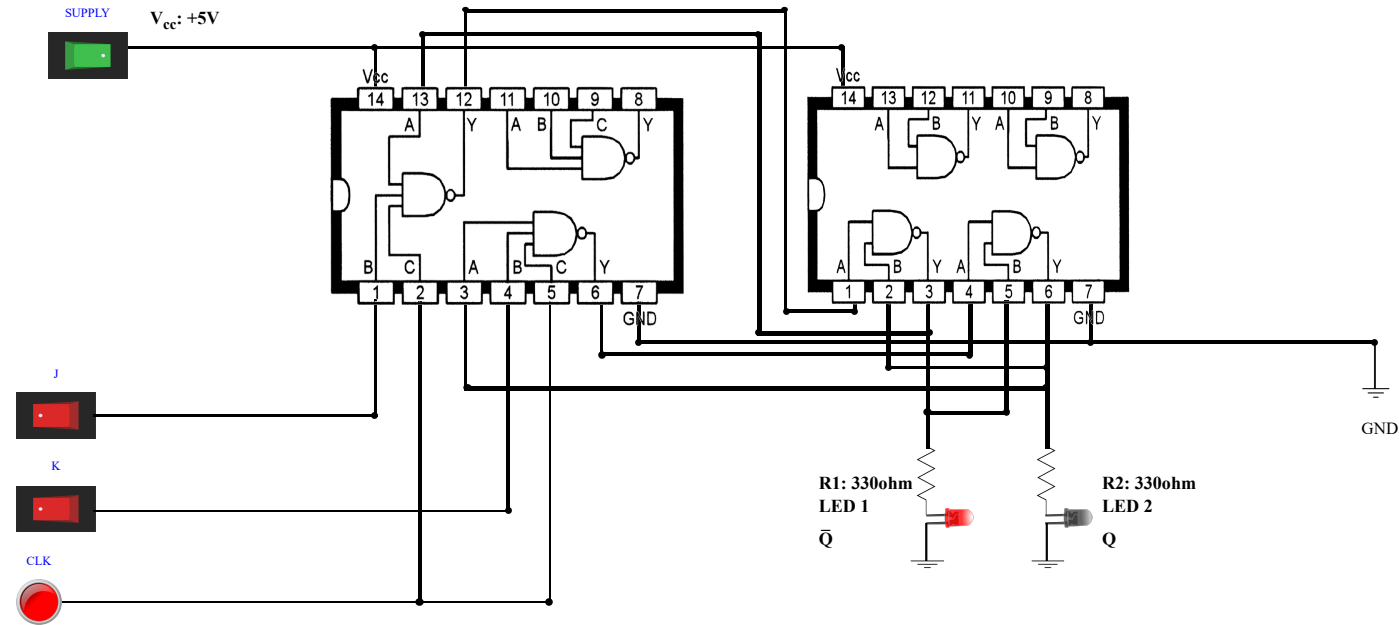


INSTRUCTIONS

Experiment to perform logic of JK FLIP FLOP on kit



TRUTH TABLE								
Serial No.	clock	J	K	Q(n-1)	Q̄(n-1)	Q	Q̄	Remark
1	1	0	0	0	1	0	1	No change
2	1	0	1	0	1	0	1	Reset
3	1	1	0	0	1	1	0	set
4	1	1	1	1	0	0	1	toggle

